


# Instrumentation: Operational Amplifiers

Medical Electrical Equipment (BME590L)

Mark L. Palmeri, M.D., Ph.D.

February 06, 2023


# BJT Differential Amplifier

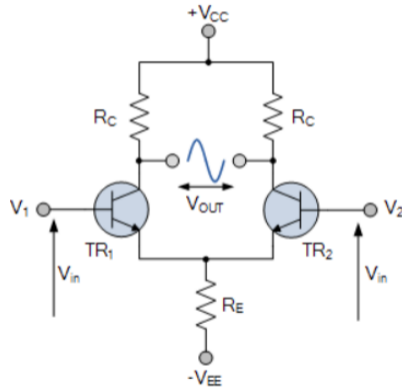

# Operational Parameters


- ▶ Common Mode Gain: Gain when  $V_1 = V_2$
- ▶ Common Mode Rejection Ratio (CMRR)

# Ideal Operational Amplifier Model

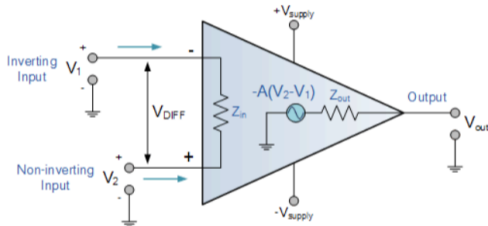

- ▶ Open Loop Gain ( $A_{VO}$ )  $\rightarrow \infty$
- ▶ Input Impedance ( $Z_{in}$ )  $\rightarrow \infty$
- ▶ Output Impedance ( $Z_{out}$ )  $\rightarrow 0$
- ▶ Bandwidth  $\rightarrow \infty$
- ▶ Offset Voltage  $\rightarrow \infty$


# Realistic Op Amps

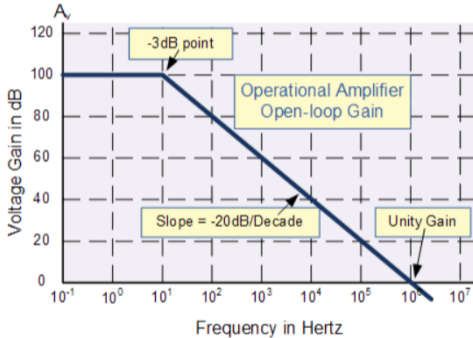


## Gain Bandwidth Product

- ▶ Output current is very limited (not a power source!)
- ▶ Output voltage limited to  $\pm$  supply voltages

# 741 Pinout

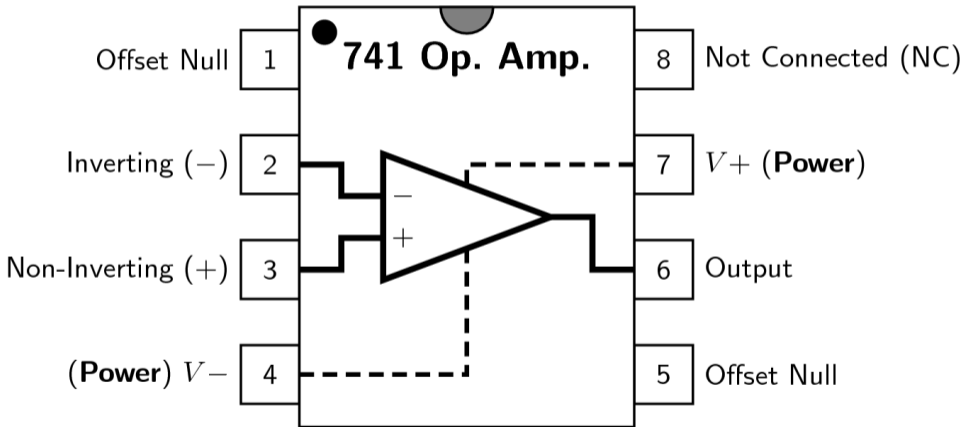


# Negative Feedback: Inverting Amplifier

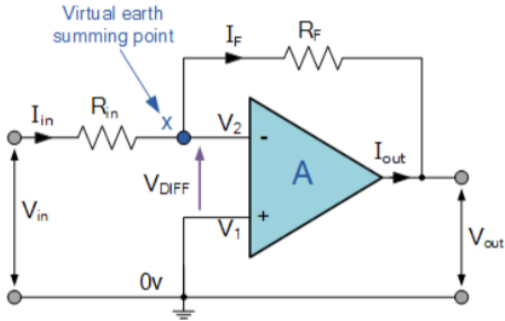


- ▶ Negative Feedback
- ▶  $V_- = V_+$
- ▶ Gain =  $\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i}$

# Transimpedance Amplifier

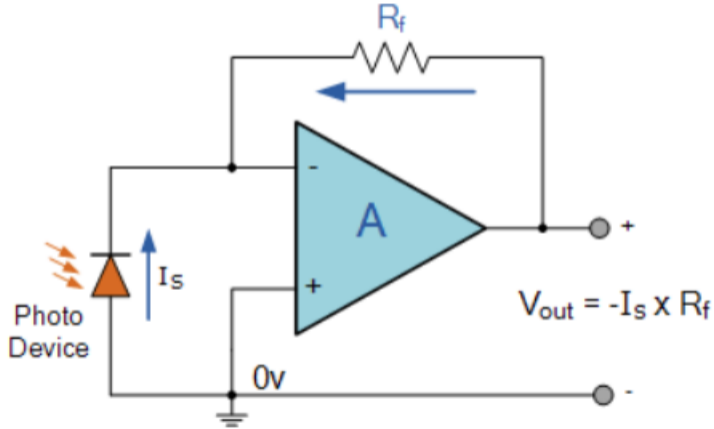





# Non-Inverting Amplifier

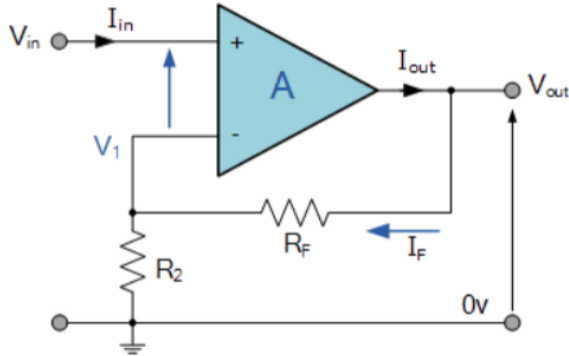

# Buffer / Follower

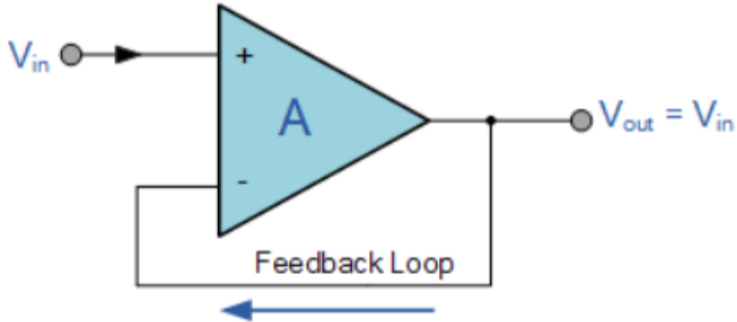


## Summing Amplifier (Inverting)

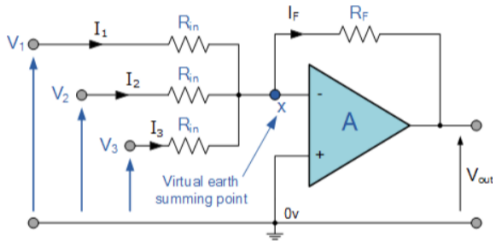


- ▶ Can weight sums with different  $R_{in}$  / branch.
- ▶  $R_f$  controls overall gain.
- ▶ Finite input impedance.
- ▶ This was the R-2R DAC!

# Audio Mixer

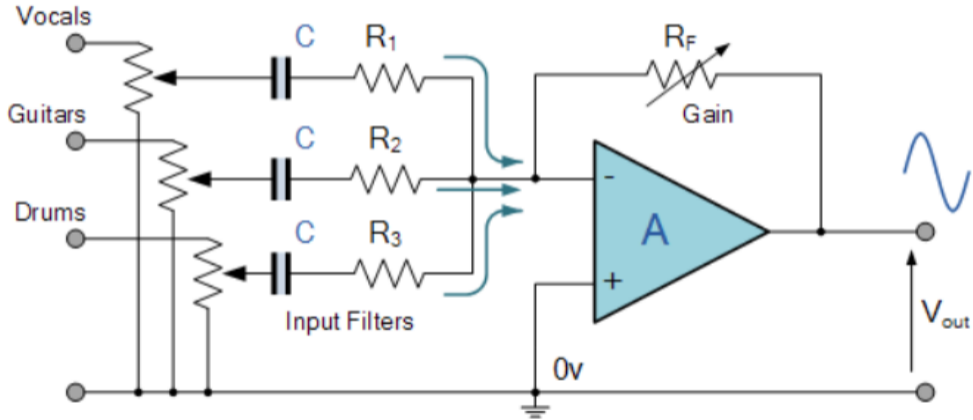


# Differential Amplifier

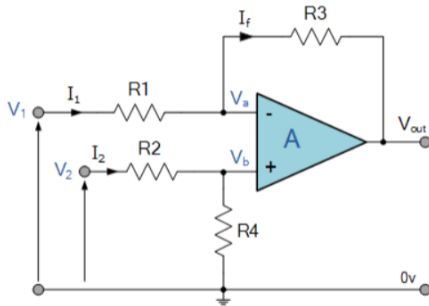


- ▶ If  $R_1 = R_2$  and  $R_3 = R_4$ ,  
$$V_{out} = \frac{R_3}{R_1}(V_2 - V_1)$$
- ▶ Finite input impedance.
- ▶ Hard to find equal pair resistors to adjust gain!

# Instrumentation Amplifier

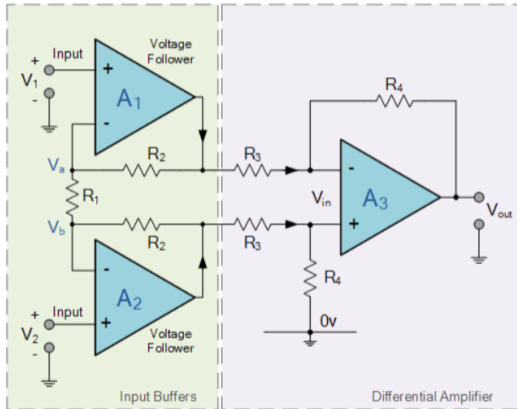


- ▶ Buffered input impedance.
- ▶ Single  $\Delta R$  gain ( $R_1$ ).
- ▶ 
$$V_{out} = (V_2 - V_1) \left[ 1 + \frac{2R_2}{R_1} \right] \left( \frac{R_4}{R_3} \right)$$

# Light-Activated Relay

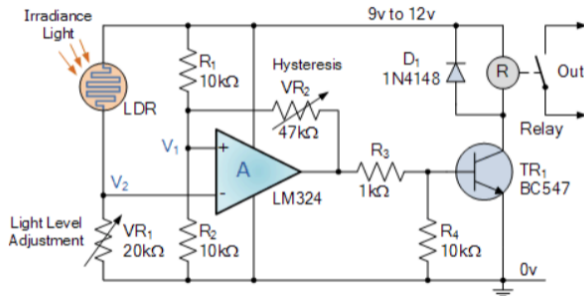



# Comparator

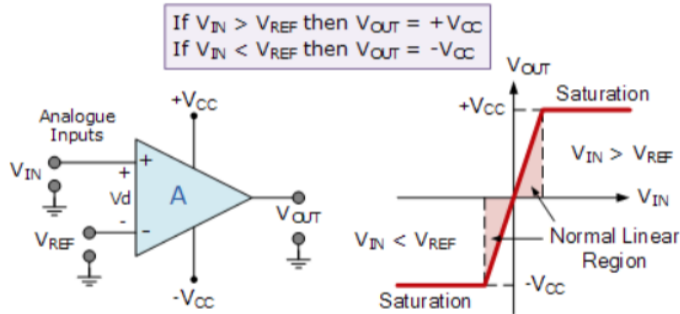


- ▶ Large open-loop gain pushed output to rails
- ▶ Remember: Flash ADC





# Schmitt Comparator (Hysteresis)

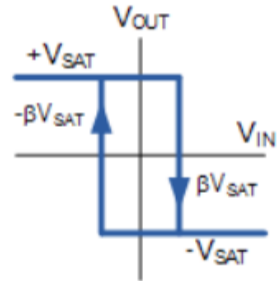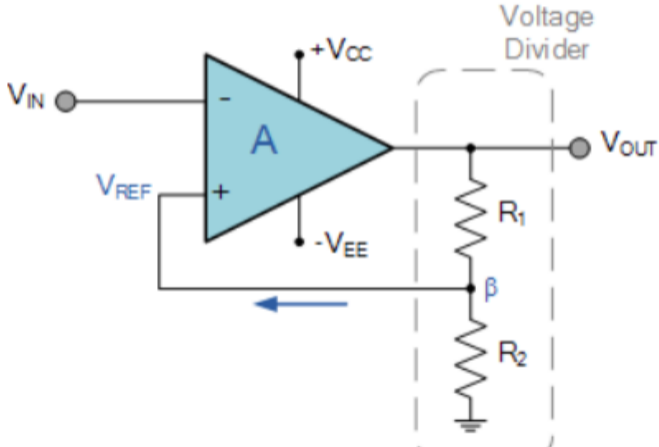

# Sine-to-Rect Converter

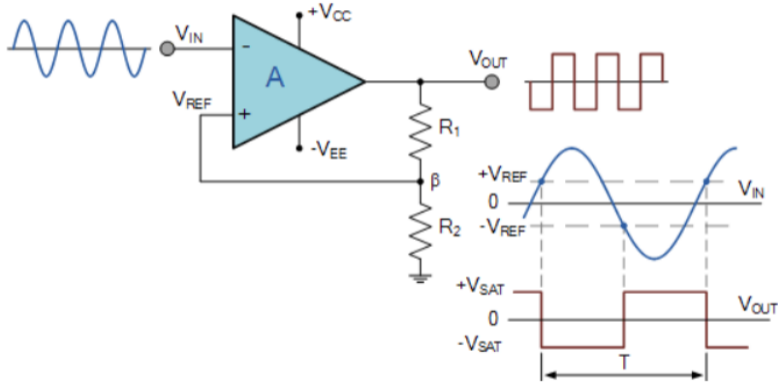

# Multivibrator

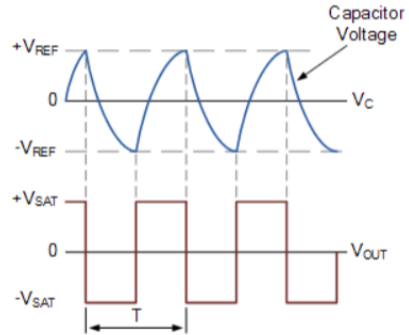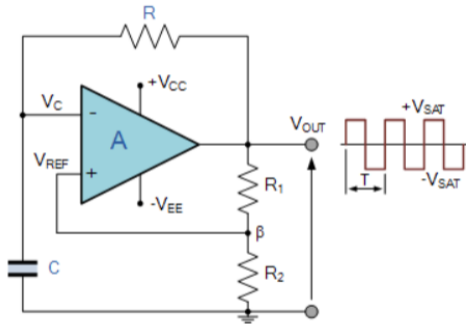

## Before next lecture...

- ▶ Read chapter on operational amplifiers.
- ▶ Make sure that you understand how all of these circuits work.

# References

- ▶ Practical Electronics for Inventors, Chapter 8 (Operational Amplifiers)
- ▶ <https://www.electronics-tutorials.ws/opamp>